

COM1006 Devices and Networks (Autumn)

COM1090 Computer Architectures

Lecture #8

Sequential Circuits

Dr Dirk Sudholt
Department of Computer Science
University of Sheffield

`d.sudholt@sheffield.ac.uk`

`http://staffwww.dcs.shef.ac.uk/~dirk/campus_only/com1006/`

Based on Chapter 3 in Clements, Principles of Computer Hardware

► Aims of this lecture


- To show how simple memory elements are implemented in digital circuits using flip-flops.
- To introduce the major kinds of flip-flops, demonstrate their behaviour and illustrate their applications.
- To introduce the concept of clocking.
- To compare level, edge and master-slave triggering.
- To show how sequential circuits can be designed with flip-flops and combinatorial logic.
- To show how flip-flops can be used to implement more complicated circuits such as shift registers and counters.

► Sequential logic

- So far we have built logic circuits using **combinatorial elements** whose outputs are a function of their inputs only.
- Now we consider **sequential circuits** whose outputs depends on their current inputs and their previous inputs.
- Example: a counter
- **Flip-flops** (also called bistables) are the building blocks of sequential circuits.
- The output of a flip-flop can remain in one of two states indefinitely, even if the input changes.
- Flip-flops are therefore basic memory elements.

► The RS flip-flop

 - The RS flip-flop is the simplest flip-flop, and consists of two **cross-coupled** NOR gates.
- We have two inputs R and S, and two outputs X and Y
- Recall the truth table for a NOR gate $\overline{P+Q}$, shown right.



| P | Q | $F = \overline{P+Q}$ |
|---|---|----------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

► Analysis of the RS flip-flop

- We can write expressions for the outputs X and Y in terms of the inputs R and S:

$$X = \overline{R+Y}$$

$$Y = \overline{S+X}$$

- Substituting for Y into the expression for X,

$$X = \overline{R + (\overline{S+X})}$$

$$= \overline{R} \cdot \overline{(\overline{S+X})}$$

by de Morgan's theorem

$$= \overline{R} \cdot (S + X) = \overline{R} S + \overline{R} X$$

- What does $X = \overline{R} S + \overline{R} X$ actually mean? The X on the RHS is the old value of X, and the X on the LHS is the new value of X. To make this clear, we can write $X^+ = \overline{R} S + \overline{R} X$

► Truth table for the RS flip-flop

- Recall $X^+ = \bar{R} S + \bar{R} X$
- If $R=1$, the output X^+ becomes 0 regardless of its previous value, and stays 0 when $R=0$
- $R=1$ causes the output to reset (become 0)**
- If $S=1$ and $R=0$, the output X^+ becomes 1 regardless of its previous value, and stays 1 when $S=0$
- $S=1$ causes the output to set (become 1)**

| Inputs | | | Output |
|--------|---|---|--------|
| R | S | X | X^+ |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

► Set and reset in the RS flip-flop

- RS flip-flops are often drawn as a “box” with inputs:

- R for reset
- S for set



- Historically the output X is labelled Q.
- Checking the original circuit, we can see that except for the case $R=S=1$, X and Y are complements. Therefore we can label the other output \overline{Q} .

❓ **Verify this by writing the truth table for $Y = \overline{S + X}$**

► A revised truth table for the RS flip-flop

- Note that the case $R=S=1$ is **forbidden**, since it implies $Q=\bar{Q}=0$
- In practice the input $R=S=1$ is simply avoided.

| Inputs | | | Output | |
|--------|---|---|--------|-----------|
| R | S | Q | Q^+ | |
| 0 | 0 | 0 | 0 | No change |
| 0 | 0 | 1 | 1 | No change |
| 0 | 1 | 0 | 1 | Set |
| 0 | 1 | 1 | 1 | Set |
| 1 | 0 | 0 | 0 | Reset |
| 1 | 0 | 1 | 0 | Reset |
| 1 | 1 | 0 | 0 | Forbidden |
| 1 | 1 | 1 | 0 | Forbidden |


► Algebraic RS flip-flop truth table

- A form of the truth table that uses the algebraic value of Q is frequently used, because it is more concise:

| Inputs | | Output | Description |
|--------|---|--------|-------------------|
| R | S | Q^+ | |
| 0 | 0 | Q | No change |
| 0 | 1 | 1 | Set output to 1 |
| 1 | 0 | 0 | Reset output to 0 |
| 1 | 1 | X | Forbidden |


► Application of the RS flip-flop

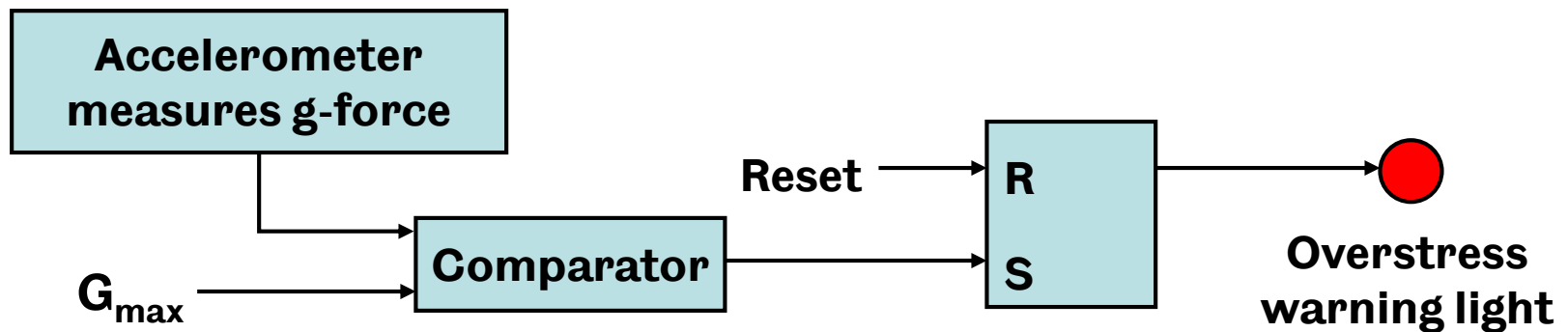- An important application of the RS flip-flop is the recording of brief events (i.e., it acts as a **latch**).
- Example: it is important to record situations in which an aircraft has been placed under high stress, even if briefly.
- This circuit uses a RS flip-flop to set a warning light if the g-force measured by an accelerometer exceeds a limit:




► Clocked flip-flops

 - In a **clocked** flip-flop, inputs are ignored while the clock signal is 0. The clock input prevents the flip-flop from acting until the right time (useful for dealing with **glitches**).
- We can make a **clocked RS-flip flop** by ANDing the R and S inputs with a clock signal:



- clock=0 means $R' = S' = 0$, ignoring R and S.
clock=1 forwards inputs signals: $R' = R$ and $S' = S$.


► The D flip-flop (D for Data / Delay)

 

- The D flip-flop consists of an RS flip-flop and a few gates.
- It is a clocked flip-flop, with data (D) and clock (C) inputs.
- When clocked, RS flip-flop is either reset ($D=0$) or set ($D=1$). This avoids $R=S=1$.

► Behaviour of the D flip-flop

 
- When a D flip-flop is clocked, the D input is transferred to the output and remains constant until the next time it is clocked.
- The D flip-flop is suitable for implementing simple memory elements; it records the state of the input and remembers it until clocked again.



| Inputs | | Output |
|--------|---|--------|
| C | D | Q^+ |
| 0 | 0 | Q |
| 0 | 1 | Q |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


► Register implemented with D flip-flops

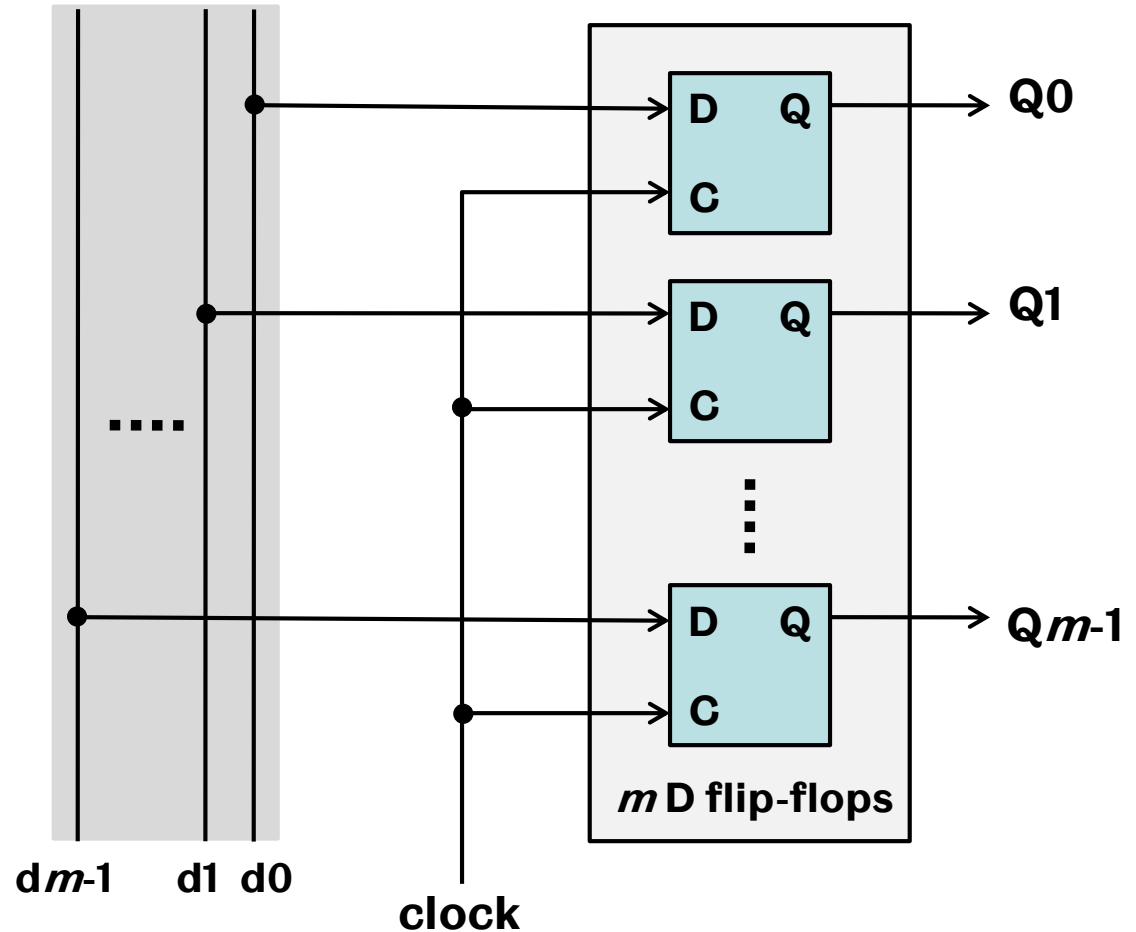- An m -bit wide bus transfers data into a register consisting of m D flip-flops.
- Bus contents are ignored when $\text{clock}=0$. Data on all m bus lines are stored when $\text{clock}=1$.




► JK flip-flop

 - Like RS flip-flop, but with additional logic avoiding $R=S=1$.
- Allows to maintain, set, clear, and toggle current state.



► Truth table for JK flip-flop

 - JK flip-flop behaves like an RS flip-flop for all values of J (set) and K (clear) except J=K=1.
- When J=K=1 the output of the JK flip-flop changes state (**toggles**) each time it is clocked.



| Inputs | | Output | Description |
|--------|---|----------------|--------------------------|
| J | K | Q^+ | |
| 0 | 0 | Q | No change |
| 0 | 1 | 0 | Clear (“ K lear”) |
| 1 | 0 | 1 | Set |
| 1 | 1 | \overline{Q} | Toggle |

► Summary of flip-flop types

- Flip-flops have internal states as well as external inputs, and therefore function as memory elements
- **RS flip-flop.** Two inputs, (R)eset and (S)et. $R=S=1$ is forbidden. It is a latch, used for recording (even transient) events.
- **D flip-flop.** Two inputs, (D)ata and (C)lock. It records the state of D and holds it constant until C is clocked. It is used for memory elements such as registers.
- **JK flip-flop.** Has three inputs, J (Set), K (Klear) and (C)lock. Output remains in previous state so long as it is not clocked. Works like RS flip-flop, but toggles if $J=K=1$.

► Clocking – level triggered

- There are actually three ways of clocking a flip-flop; **level**, **edge** and **master-slave** triggering.
- A level-sensitive flip-flop is triggered whenever the clock is in a particular logical state (0 or 1; we assume 1 hereafter).
- The clocked RS flip-flop on slide 11 is level triggered because it only responds to the R and S inputs when the clock is input is high.
- Level-triggering is unsuited to some applications (e.g., digital circuits in which the output is fed back into the input, since the state of the circuit will oscillate during a single clock pulse).

► Clocking – edge triggered


- Edge-triggered flip-flops are clocked by the transition of the clock from zero to one (**rising edge**), or one to zero (**falling edge**).




- Edge-triggered flip-flops solve many of the problems of level triggering because the transition is very short (less than 1ns).
- Clock skew (tiny variations in arrival time of pulses at each clock input) can cause a problem for edge triggering.

► Clocking - master/slave

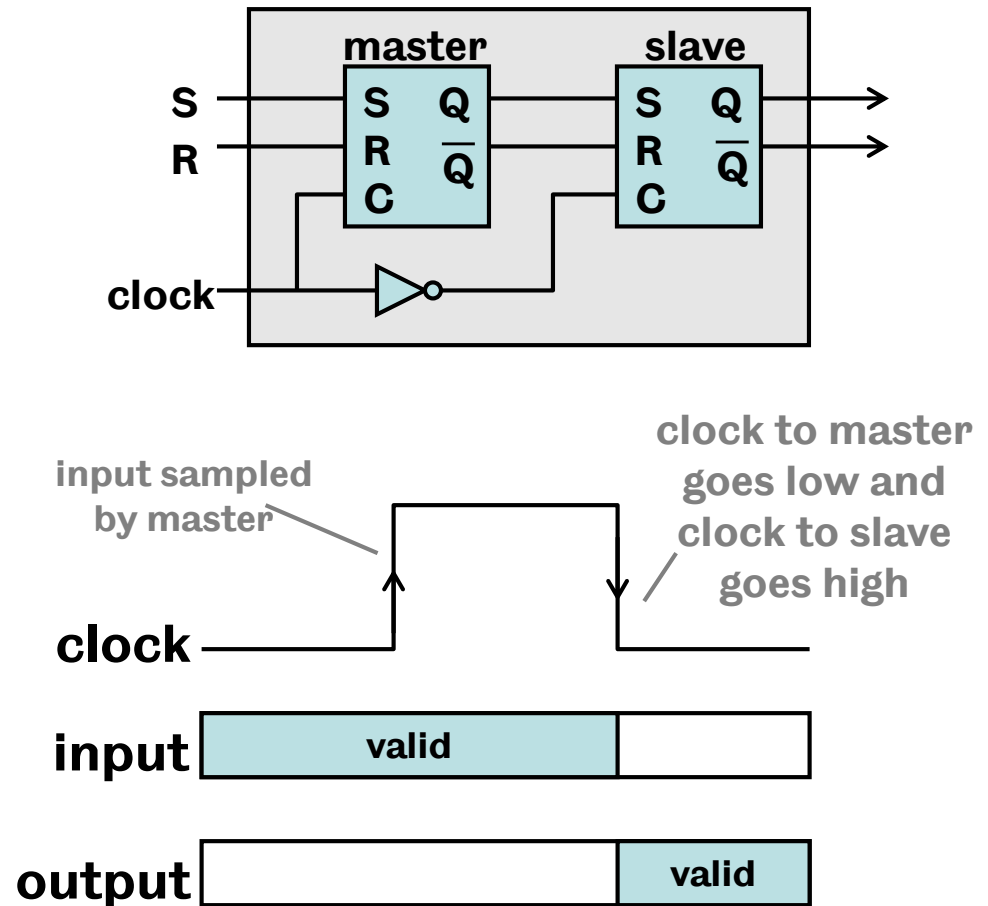- A master-slave (MS) flip-flop is actually two flip-flops operating in series. The master flip-flop captures the input, the slave flip-flop holds the output.
- Master triggers on high level, slave on low level.
- Like an air-lock in a submarine!




► Comparison of triggering behaviour

 


► How to design sequential circuits

 - States of flip-flops can be treated like regular inputs
- Combinatorial logic is used to implement outputs as well as inputs for flip-flops (J&K or R&S or D).



► Example: custom up-and-down counter

- Let's design a two-bit counter that counts 0, 2, 3 (skipping 1).
- It has a switch, an input A, determining whether to count up or down when clocked.
 - If $A=0$, the counter counts up
 - If $A=1$, the counter counts down
- Example of a **state machine** used to model sequential circuits. (loads more of this in COM2003)
- The counter never reaches „01“.
- Need two flip-flops to represent current number/state Q_1Q_0 . Any flip-flop type will do – let's choose to use two JK flip-flops.

 

► Step 1: truth table for state transitions

- Figure out how the next states need to be set, according to inputs and current state.

| Input A | Current state | | Next state | |
|------------|---------------|-------|------------|---------|
| | Q_1 | Q_0 | Q_1^+ | Q_0^+ |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | X | X |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | X | X |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

► Step 2: determine inputs for flip-flops

- New state Q_1^+ , Q_0^+ being determined by flip-flop inputs J_1 , K_1 , J_0 , K_0 .
- Work out how to set these to get the desired next state.
- Use „don't cares“ if next state is „X“.

| Input A | Current state | | Next state | | Inputs for JK-flip flops | | | |
|------------|---------------|-------|------------|---------|--------------------------|-------|-------|-------|
| | Q_1 | Q_0 | Q_1^+ | Q_0^+ | J_1 | K_1 | J_0 | K_0 |
| 0 | 0 | 0 | 1 | 0 | | | | |
| 0 | 0 | 1 | X | X | X | X | X | X |
| 0 | 1 | 0 | 1 | 1 | | | | |
| 0 | 1 | 1 | 0 | 0 | | | | |
| 1 | 0 | 0 | 1 | 1 | | | | |
| 1 | 0 | 1 | X | X | X | X | X | X |
| 1 | 1 | 0 | 0 | 0 | | | | |
| 1 | 1 | 1 | 1 | 0 | | | | |

► How to set inputs for flip-flops

- Force next state to 0 or 1 according to flip-flop's truth table.
- Depending on current state, there might be further options.
(Recall: the more „don't cares“, the better!)

| Curr. State | Next State | RS inputs | |
|-------------|------------|-----------|---|
| Q | Q+ | R | S |
| 0 | 0 | X | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | X |

| Curr. State | Next State | JK inputs | |
|-------------|------------|-----------|---|
| Q | Q+ | J | K |
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

| Curr. State | Next State | D input |
|-------------|------------|---------|
| Q | Q+ | D |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

avoid R=S=1!

► Step 2: determine inputs for flip-flops

- Here's the completed table:

| Input A | Current state | | Next state | | Inputs for JK-flip flops | | | |
|------------|---------------|-------|------------|---------|--------------------------|-------|-------|-------|
| | Q_1 | Q_0 | Q_1^+ | Q_0^+ | J_1 | K_1 | J_0 | K_0 |
| 0 | 0 | 0 | 1 | 0 | 1 | X | 0 | X |
| 0 | 0 | 1 | X | X | X | X | X | X |
| 0 | 1 | 0 | 1 | 1 | X | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 0 | X | 1 | X | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 1 | X |
| 1 | 0 | 1 | X | X | X | X | X | X |
| 1 | 1 | 0 | 0 | 0 | X | 1 | 0 | X |
| 1 | 1 | 1 | 1 | 0 | X | 0 | X | 1 |

► Step 3: design circuits for flip-flop inputs

J_1

| | | AQ_1 | | | |
|-------|---|--------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q_0 | 0 | 1 | X | X | 1 |
| | 1 | X | X | X | X |

$J_1 = 1$

K_1

| | | AQ_1 | | | |
|-------|---|--------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q_0 | 0 | X | 0 | 1 | X |
| | 1 | X | 1 | 0 | X |

$K_1 = \bar{A}Q_0 + A\bar{Q}_0$

J_0

| | | AQ_1 | | | |
|-------|---|--------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q_0 | 0 | 0 | 1 | 0 | 1 |
| | 1 | X | X | X | X |

$J_0 = \bar{A}Q_1 + A\bar{Q}_1$


K_0

| | | AQ_1 | | | |
|-------|---|--------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q_0 | 0 | X | X | X | X |
| | 1 | X | 1 | 1 | X |

$K_0 = 1$

► Step 4: assemble circuits and flip-flops

 - $Q_0, Q_1, \overline{Q_0}, \overline{Q_1}$ used as inputs to circuits for J_0, K_0, J_1, K_1
- Here: $J_1=K_0=1$ implemented by line to power
- Clock with edge triggering.
- Added 7-segment display for output.



► Synchronous & asynchronous systems

- **Synchronous system** – a clocked system in which all processes share the same clock signal. All outputs are held constant until the next time the flip-flops are clocked.
- **Asynchronous system** – the output of one process triggers the start of the next.
- Previous design method is for **synchronous systems**.
- Asynchronous systems are more complex and harder to design, but faster and use less power.
- Synchronous systems are often required due to the effect of propagation delays on digital circuits.

► Shift register

- By modifying the circuit for a register we can build a **shift register** in which the bits are moved one place right each time the register is clocked, e.g.


01110101 original contents

00111010 after clocking once

00011101 after clocking twice

- The right-most bit is lost and a zero is shifted in the left.
- If the bit pattern represents an unsigned binary number, shifting it right has the effect of **dividing** the number **by two**.

► Right shift register with D flip-flops

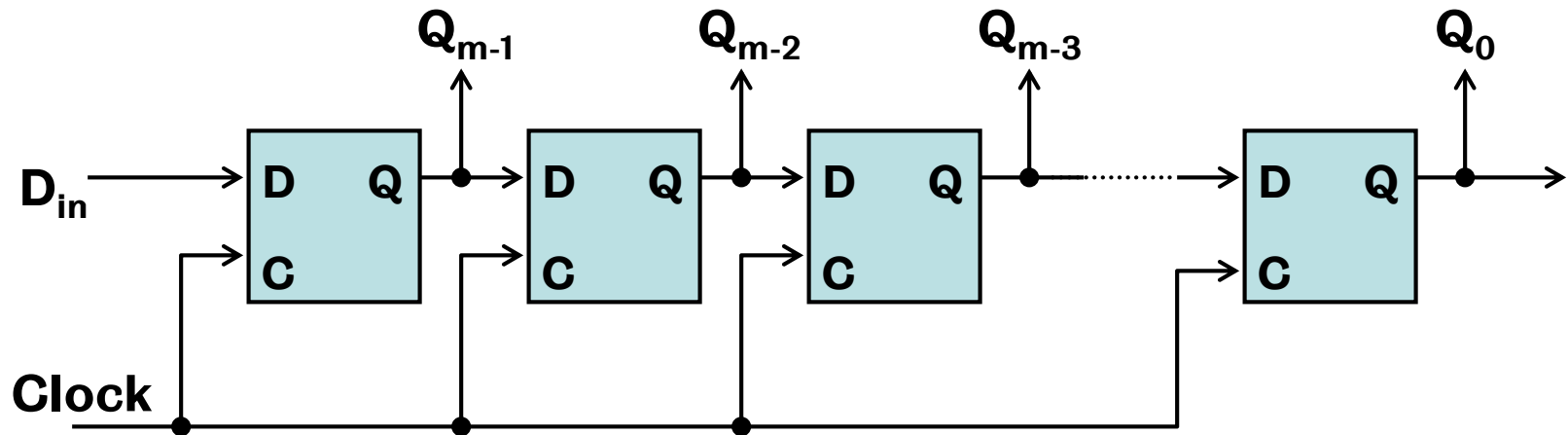


- All clock inputs are connected together so that the D flip-flops are clocked simultaneously.
- On each clock pulse the output (Q) of each flip-flop is copied to the input (D) of the next stage on the right.


❗ **Should the flip-flops be level or edge triggered?**

► Binary up-counter

 - Another example of a **state machine** to model sequential circuits.
- Implementing an ordinary 3-bit binary up-counter using a simple state machine.
- States S0-S7, each outputs the current count in the sequence.




► Asynchronous binary up-counter

 

- J and K inputs of each JK flip-flop are connected to logical 1 so that the outputs **toggle** on each clock pulse.
- Flip-flops are negative-edge triggered, change state on falling edge of the clock pulse (indicated by the circle).
- Each output triggers the next input (a **ripple counter**).

► Timing diagram for 3-bit up counter

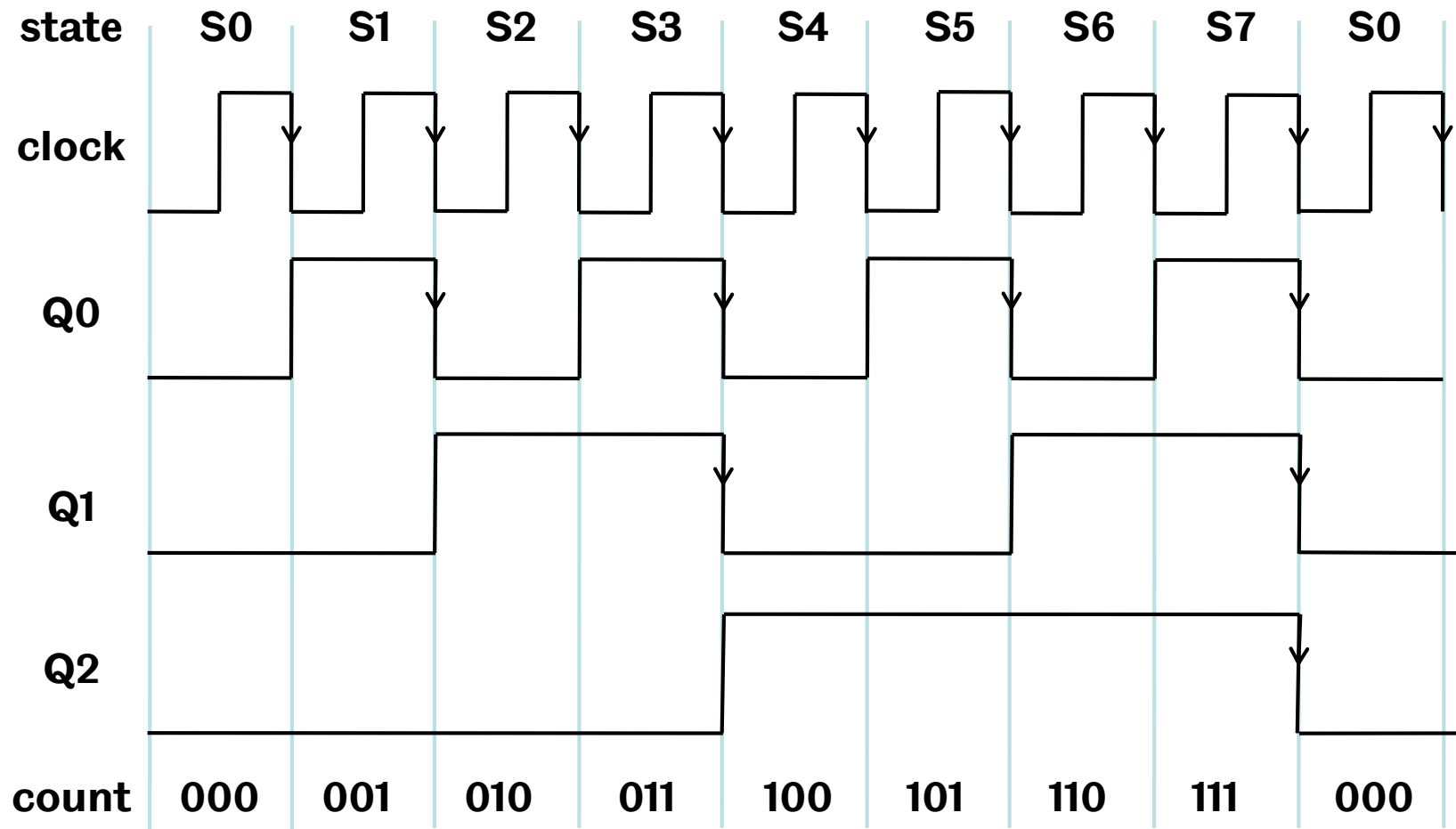

► Summary

- Flip-flops are basic memory elements.
- Different kinds of flip-flop (D, RS, JK) have different applications. JK flip-flops are the most general kind.
- Digital circuits can operate synchronously or asynchronously.
- In synchronous (clocked) circuits, the clocking can be level, edge or master-slave triggered.
- Synchronous sequential circuits can be designed with flip-flops and combinatorial logic controlling their inputs to implement the desired state transition.
- Flip-flops can be combined to make registers and shift registers.
- JK flip-flops can be used to implement simple counters.