

COM1006 Devices and Networks (Autumn)

COM1090 Computer Architectures

Lecture #4

Gates and Logic

Dr Dirk Sudholt
Department of Computer Science
University of Sheffield

`d.sudholt@sheffield.ac.uk`

`http://staffwww.dcs.shef.ac.uk/~dirk/campus_only/com1006/`

Based on parts of Chapter 2 in Clements, Principles of Computer Hardware

► Aims of this lecture

- To introduce combinatorial logic
- To introduce fundamental gates: AND, OR, NOT
- To show how truth tables can be used to describe digital circuits
- To show how a Boolean equation consisting of a sum of products can be used to describe a digital circuit
- To introduce NAND, NOR and EOR gates

► Combinatorial and sequential logic

- Digital computers are constructed from two kinds of logic elements:
- **Combinatorial logic**. Generates output based solely on its current input, e.g. if window open AND raining then close window:



- **Sequential logic** (see later lectures). The output from a sequential logic element depends on its past history as well as its current input (i.e., a sequential element remembers its previous inputs).


► Gates

- A **gate** is a simple processing element with one or more input terminals and an output terminal.
- The output of a gate is a function of its inputs only.
- Gates can be regarded as transmission elements that control the flow of information through a computer.
- Digital computers consist of nothing more than the interconnection of **AND**, **OR** and **NOT** gates.
- Other gates (**NAND**, **NOR**, **EOR**) can be derived from them.
- Later we'll see that any digital circuit can be designed from interconnected NAND (or NOR) gates alone.
- At the chip level, gates are implemented by transistors.


► Circuit conventions

- Logic circuits are generally read from left to right (i.e., inputs on left, outputs on right).
- Circuits can contain many signal paths (lines) and sometimes these must be drawn as crossing one another:

 Two lines that
cross but are
not connected



 
Two lines are
connected
(indicated by dot at
intersection)




- The voltage at any point along a conductor is constant, so the logical state is the same everywhere on a line.

► Fundamental gates: AND

 - An AND gate has two or more inputs and a single output.
- The output of an AND gate is true iff each of its inputs is true.



Two-input AND gate

 

Three-input AND gate

- The logical symbol for AND is a dot, so A AND B is written $A \cdot B$; in practice the dot is often omitted and we write AB .
- Alternative notations: $A \wedge B$, $A.B$
- Logical AND behaves like a multiplier in conventional algebra, e.g. $A(B+C) = AB+AC$ in conventional and Boolean algebra.

► Truth tables

- Truth tables are a useful way of describing the relationship between inputs and outputs of a gate.
- The value of each output is tabulated for every possible combination of the inputs.
- Inputs are binary so a circuit with n inputs has 2^n rows in its truth table.

Truth table
for the AND gate

| A | B | F = AB |
|---|---|--------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

► Logical operations on words


- Recall that computers process groups of bits called **words**. Typically a word consists of 8, 16, 32 or 64 bits.
- When logical operations such as AND are applied to words, the operation is applied to each pair of bits:

| | | | | | | | | |
|-------|---|---|---|---|---|---|---|-----------------|
| 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | word A |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | word B |
| <hr/> | | | | | | | | |
| 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | $C = A \cdot B$ |


- This example shows a common use of AND; word B acts as a **mask** that **clears** some bits of word A.

► Fundamental gates: OR

 - An OR gate has two or more inputs and a single output.
- The output of an OR gate is true if any one (or more than one) of its inputs is true.



Two-input OR gate

 

Three-input OR gate

- The logical symbol for OR is +, so A OR B is written $A+B$.
- Alternative notation: $A \vee B$
- The logical OR operator behaves like addition in conventional algebra.

❓ Does logical OR have the same meaning as “or” in English?

► Truth table and logical OR on words

- Computers also perform logical OR on words, e.g.:

| | | | | | | | | |
|-------|---|---|---|---|---|---|---|--------|
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | word A |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | word B |
| <hr/> | | | | | | | | |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | C=A+B |

- Logical OR is used to **set** one or more bits in a word to logical 1.
- So using AND and OR we can selectively set and clear the bits of a word.


Truth table for
the OR gate

| A | B | F = A+B |
|---|---|---------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

► AND and OR gates as circuits


AND

 Current will only flow
if A and B are closed




OR

 Current will flow if
either A or B is closed



► Fundamental gates: NOT

 - The NOT gate is also called an **inverter** or **complementer**.
- The NOT gate has one input and one output. The output is the opposite (logical inverse) of the input.



NOT gate


| A | F = \bar{A} |
|---|---------------|
| 0 | 1 |
| 1 | 0 |

Note that it's the small circle that indicates logical inversion, not the triangle

- Other conventions: A^* , $\neg A$, $/A$
- NOT can also be applied to words (e.g., if $A=11011100$ then $\bar{A} = 00100011$)

► Example of AND-OR-INVERT logic

 - Problem: construct a 3-input majority device. The output is to be TRUE when 2 or more of the inputs are TRUE.



- General approach:
 - Construct a **truth table** that defines the required behaviour;
 - Read a **sum of products** expression from the truth table
 - **Simplify** the expression in order to minimise the number of gates/lines used (just examples now; see later lectures)
 - **Construct** the device (on paper or in a simulator)

► Step 1: Truth table

Note that when tabulating the possible values of the inputs the order is not important, but it is usual to list them in the natural binary sequence

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

► Step 2: Sum of products expression

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

- From the truth table, we can write down the set of inputs that cause the output to be true:
 $\bar{A}BC, A\bar{B}C, AB\bar{C}, ABC$
- The output F is the logical sum of these four cases:
$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$
- This is called a **sum of products (S-of-P) expression** because it is the logical OR (sum) of a group of terms each composed of several variables ANDed together (products)
- Useful for drawing circuits in a systematic fashion (see later)

► Sum of products expression (continued)

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

- The terms $\bar{A}BC$, $A\bar{B}C$, $AB\bar{C}$, ABC represent **minterms**.
- A **minterm** is a product of all variables in true or complemented form.
- **Every** Boolean function F can be described as sum of products (i.e. ORing minterms where F is 1).
- This is called **canonical form**.
- So every Boolean function can be implemented with AND, OR, NOT.
- There is an alternative representation based on **products of sums (P-of-S)**, ANDing sums of variables where F is 0.

► Step 3: Simplify the S-of-P expression

- We have $F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
- There is a simpler form for this expression, using fewer and simpler terms.

❓ Why do you think a simpler form is better?

- We'll spend the next lecture talking about how to simplify expressions.
- For now, I'll give the solution away – a simpler form is:

$$F = AB + BC + AC$$


- How can you be sure that it's the same function?

► Comparing Boolean Functions


| A | B | C | F | $AB + BC + AC$ |
|---|---|---|---|----------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

- Two Boolean functions are equal if all entries in the truth table are the same.
- This method is not feasible for many variables.

► Step 4: Construct the device

 

► Step 4: Construct the device

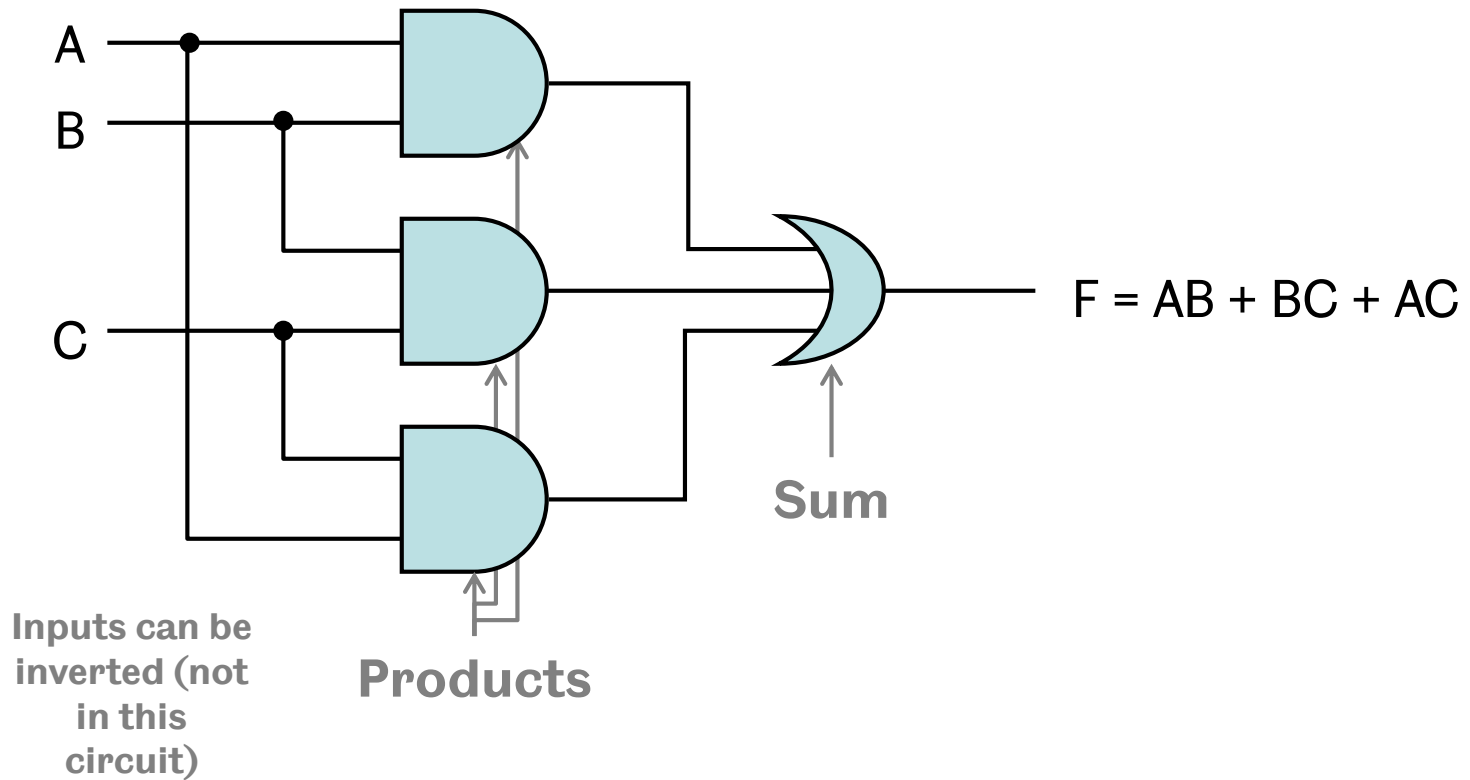


► **NAND and NOR gates**

- NAND and NOR gates are the two most widely used gates in real circuits.
- They are not fundamental gates because they are derived from the other gates we've seen:
 - The NAND gate is derived from an AND gate followed by an inverter (Not AND)
 - The NOR gate is derived from an OR gate followed by an inverter (Not OR)
- Remember that the small circle indicates inversion.
- Another common gate is Exclusive OR (EOR) which is derived from AND, OR and NOT gates.

► NAND


NAND gate

 

Truth table for
the NAND gate


| A | B | $F = \overline{A \cdot B}$ |
|---|---|----------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

AND gate followed by an inverter

 

► NOR


NOR gate

 

Truth table for
the NOR gate


| A | B | $F = \overline{A + B}$ |
|---|---|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

OR gate followed by an inverter

 

► EOR


EOR gate

 

Truth table for
the EOR gate

| A | B | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


Circuit implementation of EOR gate

 

Note from the truth table that EOR is
a 1-bit adder (excluding the carry)

► Another example - what is it?

 - Consider the following digital circuit which has three inputs, one output and three intermediate values.
- What does it do?



► Truth table (incomplete)


| Inputs | | | Intermediate values | | | Output |
|--------|---|---|---------------------|-------------------|-------------------|-------------------|
| X | Y | Z | $P=\overline{X}$ | $Q=\overline{P}Y$ | $R=\overline{X}Z$ | $F=\overline{Q}R$ |
| 0 | 0 | 0 | | | | |
| 0 | 0 | 1 | | | | |
| 0 | 1 | 0 | | | | |
| 0 | 1 | 1 | | | | |
| 1 | 0 | 0 | | | | |
| 1 | 0 | 1 | | | | |
| 1 | 1 | 0 | | | | |
| 1 | 1 | 1 | | | | |

► Truth table

| Inputs | | | Intermediate values | | | Output |
|--------|---|---|---------------------|-------------------|-------------------|-------------------|
| X | Y | Z | $P=\overline{X}$ | $Q=\overline{P}Y$ | $R=\overline{X}Z$ | $F=\overline{Q}R$ |
| 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |

► It's a multiplexer (switch)

 - From the truth table, note that:
 - when $X=0$, $F=Y$
 - when $X=1$, $F=Z$
- So this circuit acts as an electronic switch, that connects the output to one of the two inputs (Y or Z) depending on the value of X:



- This circuit is called a **multiplexer**.

► Two equivalent Boolean functions

- From the truth table, we get a S-of-P expression for F:

$$F = \bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XYZ$$

- From the circuit we could also get an equation for F by writing the outputs of each gate in terms of its inputs:

$$F = \overline{QR}, Q = \overline{YP}, P = \bar{X}$$

$$\text{Therefore } Q = \overline{Y\bar{X}} \text{ by substituting for } P$$

$$R = \overline{XZ}$$

$$\text{Therefore } F = \overline{\overline{Y\bar{X}} \overline{XZ}}.$$

- So a given Boolean function can be written in more than one way; we return to this point in the next lecture.

► Summary

- Fundamental gates are AND, OR and NOT
- Digital circuits can be conveniently described by
 - A truth table
 - A Boolean function in sum-of-products form
- Fundamental gates can be used to construct three other very important gates: NAND, NOR and EOR
- The Boolean function that describes a circuit can be written in many forms; some are more amenable to implementation than others