

# **COM1006 Devices and Networks (Autumn)**

## **COM1090 Computer Architectures**

Lecture #11

### **The structure of the CPU**

Dr Dirk Sudholt  
Department of Computer Science  
University of Sheffield

`d.sudholt@sheffield.ac.uk`

`http://staffwww.dcs.shef.ac.uk/~dirk/campus\_only/com1006/`

Based on Chapter 7 in Clements, Principles of Computer Hardware

## ► Aims of this lecture


- To bridge the gap between digital logic and the instruction set architecture.
- To illustrate information flow on address paths and data paths in a simple CPU.
- To show how a computer converts an instruction opcode into actions that implement the opcode.
- To show how instructions are executed by control unit within the CPU.

## ► Instruction execution

- This lecture bridges the gap between the instruction set architecture and digital circuits: we show how a computer instruction is **executed**.
- Assume a **one-and-a-half address architecture** in which one operand is in memory and the other is a register (the Motorola 68K is one such example).
- Consider the CPU in stages, adding more detail as we proceed.
- Highly simplified: show how instructions are executed from start to finish, but modern computers **overlap** the execution of instructions (pipelining – see later).

 
# ► Information flow in the computer

- Three kinds of information flow:
  - **address paths** by which addresses flow from one part of the CPU to another
  - **data paths** by which instructions, constants, variables stored in memory and register flow
  - **control paths** which trigger events, provide clocks, control the flow of data and addresses



- First we consider address paths.
- Initially focus on the **fetch** phase of the fetch-execute cycle in which an instruction is read from memory.

## ► CPU address paths

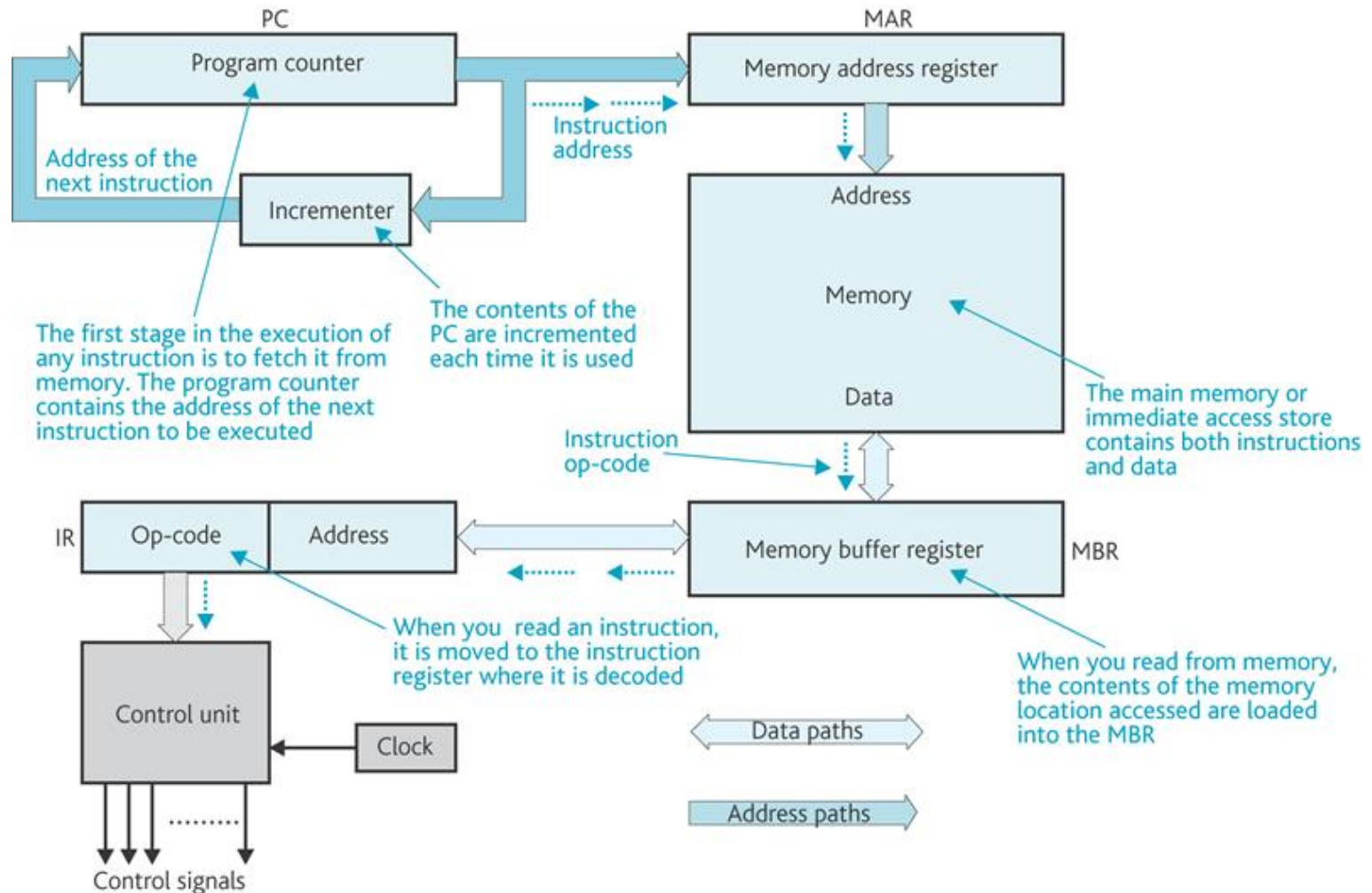

## ► Reading the instruction: registers etc.

- **Program counter** (PC) points to the next instruction to be executed.
- **Memory address register** (MAR) hold address of memory location into which data is being written in a write cycle, or from which data is being read during a read cycle.
- **Memory buffer register** (MBR) temporary holding place for data that is read from, or written to, memory.
- **Instruction register** (IR) contains instruction which is split into two fields, the operation code (**opcode**) and **operand** field (address or constant).
- **Control unit** (CU) takes opcode and stream of clock pulses and generates signals to control the CPU.

## ► Fetch phase summarised in RTL

$[MAR] \leftarrow [PC]$

Copy contents of PC to MAR.

$[PC] \leftarrow [PC] + 4$

Increment contents of PC so that it points to the next instruction to be executed.

$[MBR] \leftarrow [[MAR]]$

MAR contains copy of (previous) PC. A **memory read cycle** is performed that reads the instruction from address pointed to by MAR into the MBR.

$[IR] \leftarrow [MBR]$


Instruction is moved from MBR to IR, where it is divided into opcode and address.

$CU \leftarrow [IR_{(opcode)}]$

Opcode is copied to CU which coordinates execution of instruction (e.g., by ALU)

Note: assumes that instructions are all 32 bits long. This is true of RISC but not CISC processors such as 68K and Pentium which have variable length instruction formats.

# ► CPU data paths

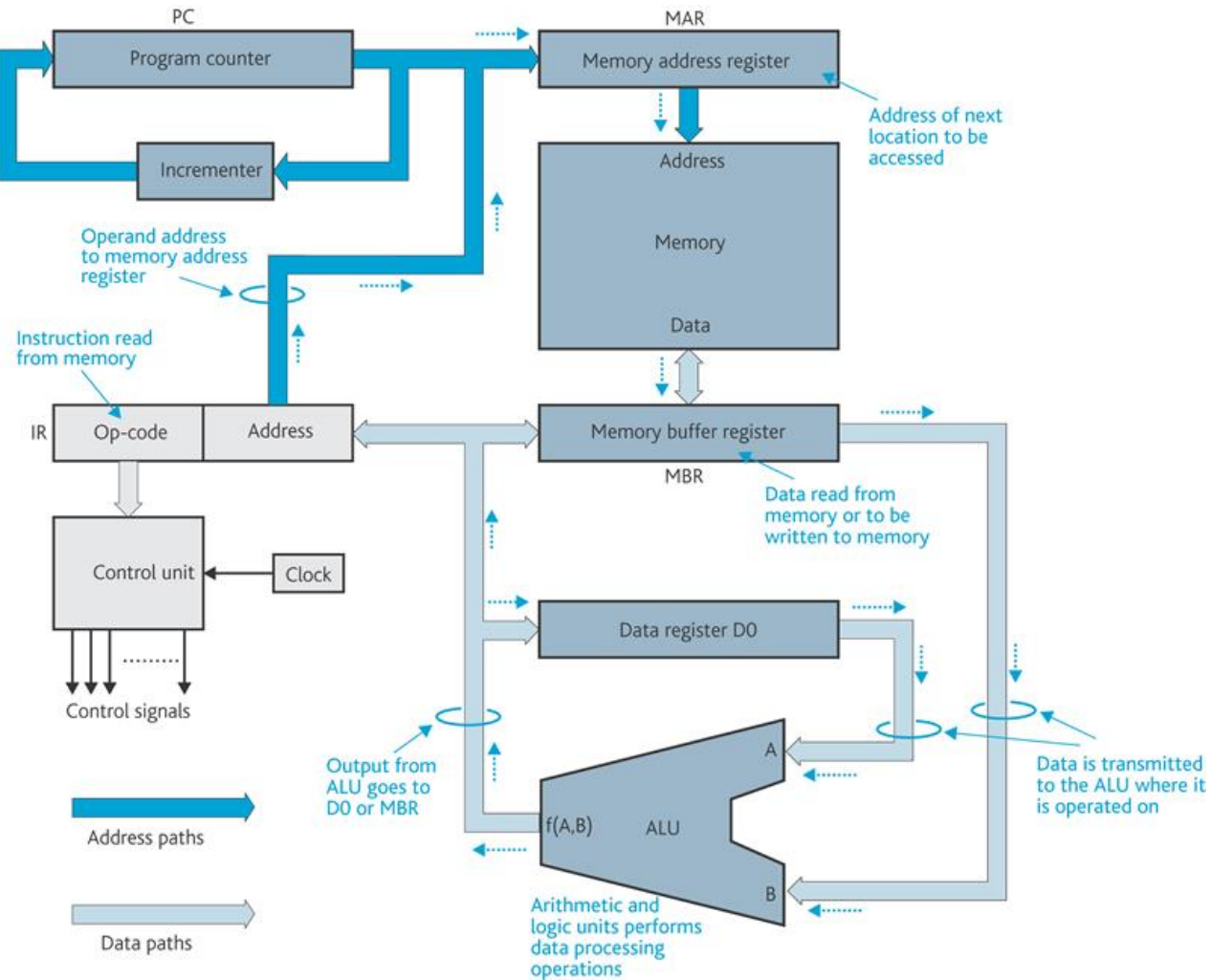



## ► Explaining the data paths

- **Data register** holds temporary results during a calculation. Called D0 for compatibility with 68K.
- Also called the **accumulator** (A) in one-address machines.
- CPU design can be easily extended to multiple registers.
- **Arithmetic and logical unit** (ALU) carries out calculations. Takes input and directs output to/from D0 and/or MBR.

## ► Execution of ADD P, D0 ( $[D0] \leftarrow [D0] + [P]$ )

FETCH  $[MAR] \leftarrow [PC]$

$[PC] \leftarrow [PC] + 4$

$[MBR] \leftarrow [[MAR]]$

$[IR] \leftarrow [MBR]$

$CU \leftarrow [IR_{(opcode)}]$

} See slide 7

ADD  $[MAR] \leftarrow [IR_{(address)}]$

$[MBR] \leftarrow [[MAR]]$

$ALU \leftarrow [MBR], ALU \leftarrow [D0]$

$[D0] \leftarrow ALU$

Move operand address to MAR

Read data from memory


Perform the addition (two operations are executed simultaneously)

Move result to data register

## ► Executing conditional instructions

- So far we've considered sequential flow of control; also need to implement **conditional branches** and **jumps** such as BNE Loop.
- To do this we need:
  - Condition code register (CCR) or processor status register. Records the carry, negative, zero and overflow flag bits.
  - A path between the CCR and the control unit so that instructions can interrogate the CCR.
  - A path between the address field of the instruction register and the program counter so that the PC can be changed as the result of a branch or jump instruction.
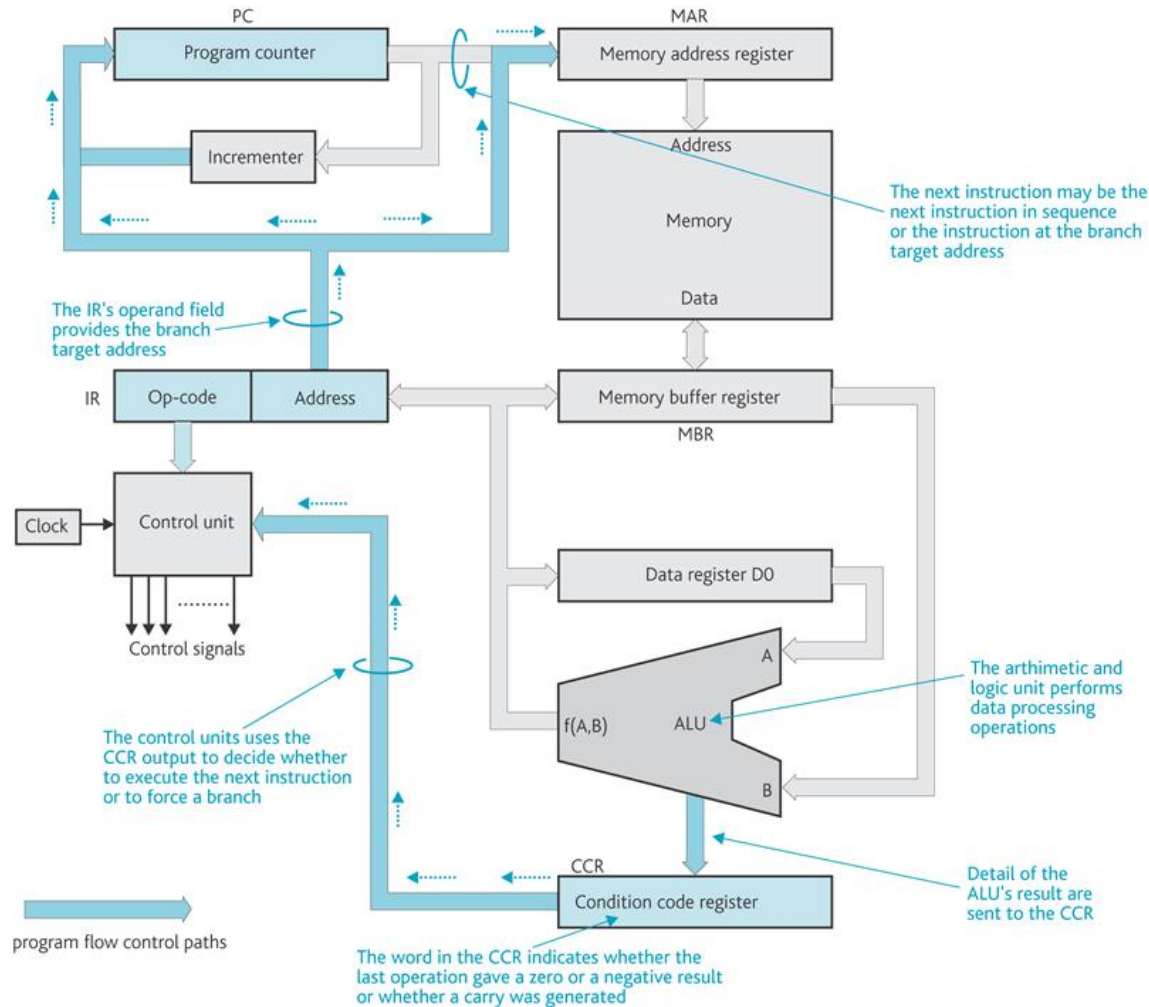
## ► Info paths for conditional instructions



## ► Example: conditional instruction

- A conditional branch instruction tests a status bit of the CCR. Then either
  - The next instruction is fetched in the usual way, **or**
  - The next instruction is obtained from the location whose **target address** is in the instruction register.
- Example: Branch on equal to zero (jump to target address if the Z-bit in the CCR is 1)
- In RTL:

BEQ target: IF [Z]=1 THEN [PC]  $\leftarrow$  [IR<sub>(address)</sub>]

## ► Dealing with literal operands

- Sometimes a literal operand value is supplied (this is indicated as part of the opcode).
- This requires a data path between the operand field of the IR and the data register for instructions such as


MOVE #30, D0                       $[D0] \leftarrow 30$

and a data path between the operand field of the IR and the ALU for instructions such as

ADD #12, D0                       $[D0] \leftarrow [D0] + 12$

- The schematic CPU shown next is essentially complete; it can execute any computer program (but enhancements can improve performance, such as adding more registers).

# ► Complete schematic of simple CPU

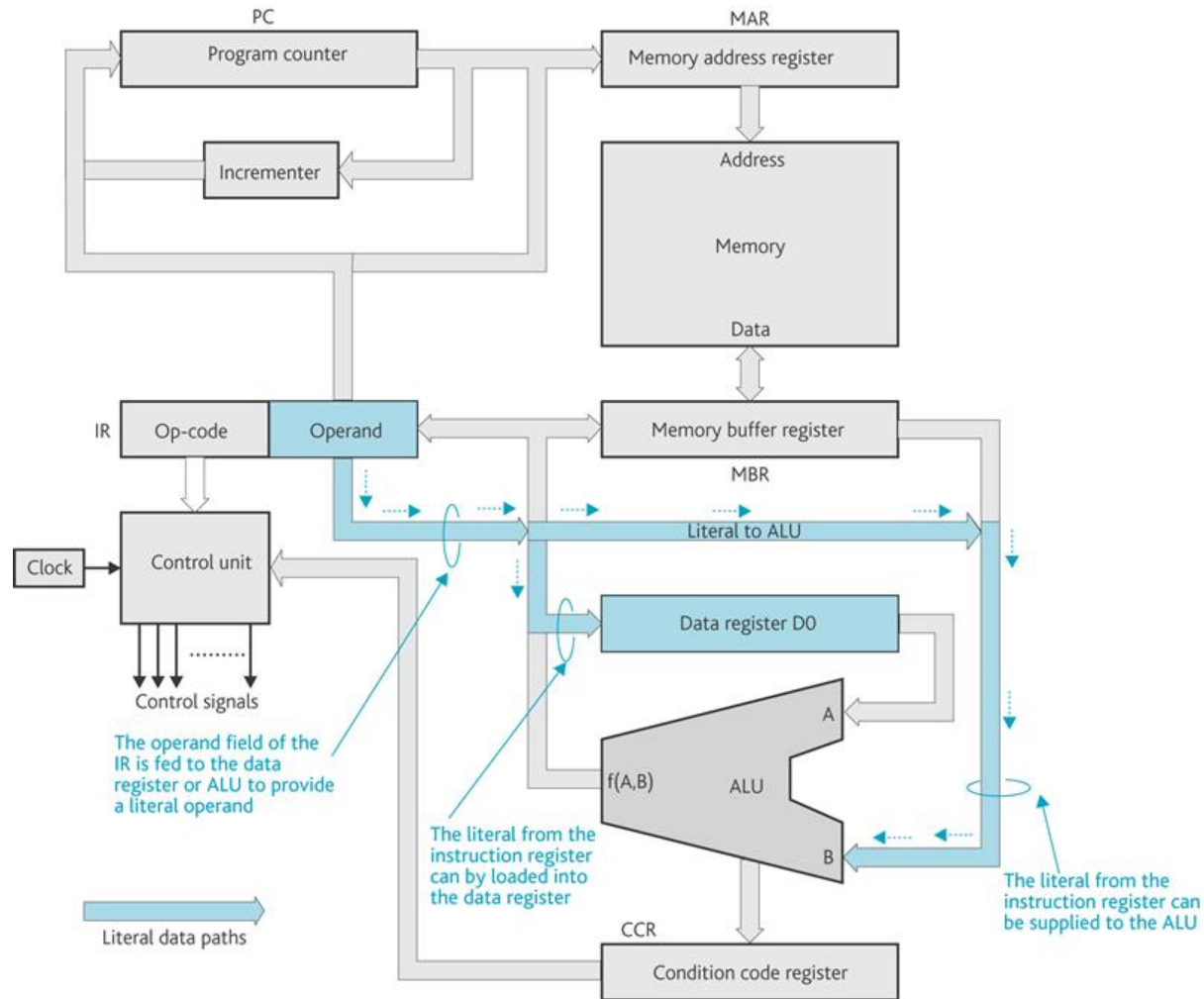


## ► How is an instruction executed?

- How is a binary pattern (e.g.,  $1101101110101001_2$ ) turned into a sequence of machine-level instructions that cause an instruction (e.g., ADD P, D0) to be executed?
- Control unit provides logic that directly transforms instructions into control signals (**random logic control unit**)
- **Random** logic control unit implies that arrangement of gates is **specific** for a particular computer.
- Opcode is decoded by a **demultiplexer**.
- To illustrate a random control unit, we consider a primitive CPU and the control signals needed to operate it.



# ► Simple single-bus CPU

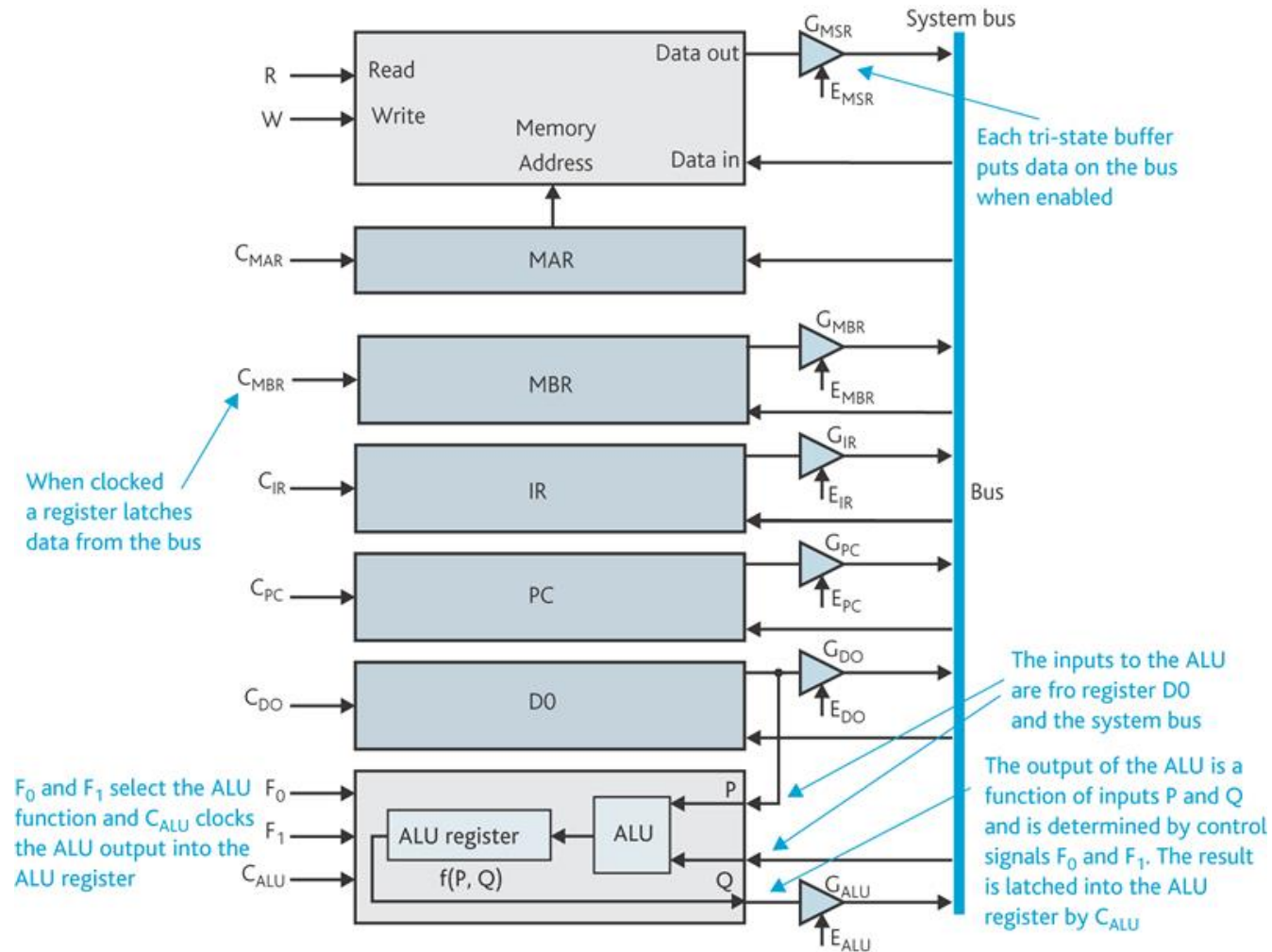

## ► Information flow in the simple CPU

- Simple CPU with bus connecting registers and memory.
- Memory receives address of location to be accessed from MAR. Note that data can be transferred directly to register from memory (not only via MBR).
- ALU has two inputs (P from D0, Q from bus).
- ALU controlled by a two-bit code ( $F_0$  and  $F_1$ ), e.g. 00 → add P to Q, 01 → subtract Q etc. ALU has an internal register.
- When tri-state gates (e.g.,  $G_{MSR}$ ) are enabled, data flows from memory or register onto bus.
- Data is copied from bus to register by clocking it (e.g.,  $C_{IR}$ )

## ► Control signals in the simple CPU

Signal	Type	Operation
R, W	Memory control	Read from / write to memory
C <sub>MAR</sub>	Register clock	Clock data into MAR
C <sub>MBR</sub>	Register clock	Clock data into MBR
C <sub>PC</sub>	Register clock	Clock data into program counter
C <sub>IR</sub>	Register clock	Clock data into instruction register
C <sub>D0</sub>	Register clock	Clock data into data register
C <sub>ALU</sub>	Register clock	Clock data into ALU register
E <sub>MSR</sub>	Bus control	Gate data from memory onto the bus
E <sub>MBR</sub>	Bus control	Gate data from MBR onto the bus
E <sub>IR</sub>	Bus control	Gate operand from IR onto the bus
E <sub>PC</sub>	Bus control	Gate program counter onto the bus
E <sub>D0</sub>	Bus control	Gate data register onto the bus
E <sub>ALU</sub>	Bus control	Gate ALU function register onto the bus
F <sub>0</sub> , F <sub>1</sub>	ALU control	Select ALU function

## ► Example: Implementing LOAD N

- Consider a LOAD N instruction  $[D0] \leftarrow [N]$ .
- First we define the operations (in RTL) needed to perform this instruction

$[MAR] \leftarrow [IR]$       copy target address (N) from IR to MAR

$[D0] \leftarrow [[MAR]]$       copy data at target address to data register

- Now consider the control signals needed to implement each step in the simple CPU:


$[MAR] \leftarrow [IR]$        $E_{IR}=1, C_{MAR}=1$

$[D0] \leftarrow [[MAR]]$        $R=1, E_{MSR}=1, C_{D0}=1$

- Combine with **timing signals** to do things at the right time.
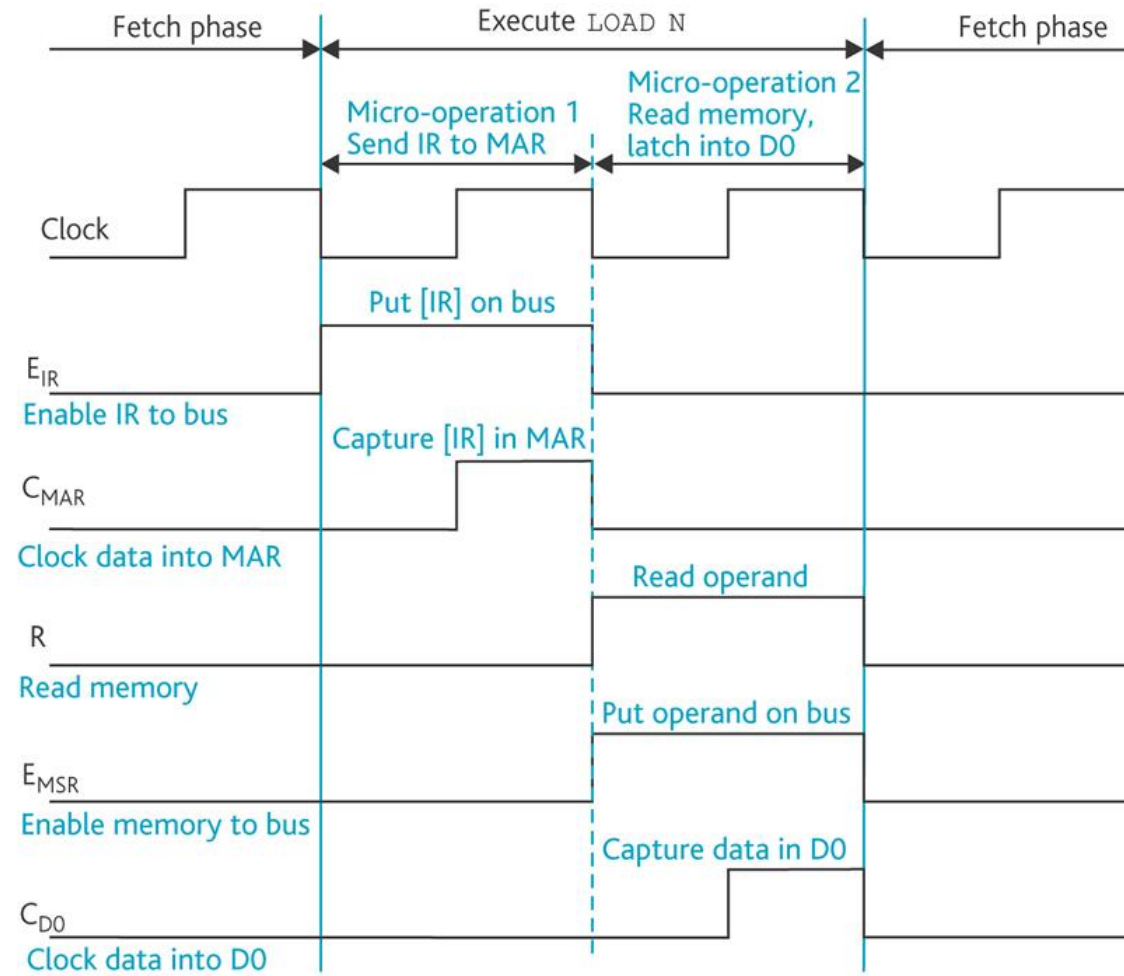
## ► Timing of the execute phase of LOAD N

Note: other control signals are not shown because they do not play a role in the execution of the LOAD N instruction



## ► Summary

- Learned how information flows in a CPU.
- The CPU consists of
  - data paths and address paths
  - registers and an interface to memory (MAR, MBR)
  - an arithmetic logic unit (ALU)
  - a control unit which controls clock signals and data paths.
- An instruction (c.f. assembly language mnemonic) is implemented by a sequence of microinstructions.
- Instructions have a fetch cycle and an execute cycle.
- A random logic control unit implements macroinstructions directly in digital logic.