

# **COM1006 Devices and Networks (Autumn)**

## **COM1090 Computer Architectures**

Lecture #5

### **Simplifying Circuits**

Dr Dirk Sudholt  
Department of Computer Science  
University of Sheffield

`d.sudholt@sheffield.ac.uk`

`http://staffwww.dcs.shef.ac.uk/~dirk/campus\_only/com1006/`

Based on Section 2.5 in Clements, Principles of Computer Hardware

## ► Aims of this lecture

- To introduce Boolean algebra
- To show how Boolean algebra can be used design and simplify logic circuits
- To introduce Karnaugh maps as a visual aid in simplifying logic circuits
- To show how digital circuits can be implemented in NAND and NOR logic only

## ► Boolean algebra

- George Boole (1815-1864) was an English mathematician and philosopher.
- He developed a logical calculus of truth values, which at the time was a relatively obscure work.
- Subsequently Claude Shannon and others showed how Boolean algebra could be used to implement logic in electrical switches.



## ► Laws of Boolean algebra

- **Commutative law:** AND and OR operators are commutative so the order of the variables in a sum or product group doesn't matter:

$$A+B = B+A$$

$$A \cdot B = B \cdot A$$

- **Associative law:** AND and OR are associative so the order in which sub-expressions are evaluated doesn't matter:

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$A+(B+C) = (A+B)+C$$

- **Distributive law:** AND behaves like multiplication and OR behaves like addition. In an expression containing both AND and OR operators, AND takes precedence over OR:

$$A \cdot (B+C) = A \cdot B + A \cdot C$$

$$(A \cdot B)+C = (A+C) \cdot (B+C)$$

## ► Boolean identities

AND	OR	NOT
$0 \cdot X = 0$	$0 + X = X$	$\overline{\overline{X}} = X$
$1 \cdot X = X$	$1 + X = 1$	
$X \cdot X = X$	$X + X = X$	
$X \cdot \overline{X} = 0$	$X + \overline{X} = 1$	

## ► Combining minterms

- For every Boolean formulas  $X$  and  $Y$  we have


$$\begin{aligned} & XY + X\bar{Y} \\ &= X(Y + \bar{Y}) \quad (\text{distributive law}) \\ &= X \cdot 1 \quad (\text{as } Y + \bar{Y} = 1) \\ &= X \quad (\text{as } X \cdot 1 = X) \end{aligned}$$

- This is a useful tool for simplifying an S-of-P expression.
- Example:  $F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$  from the majority circuit.
- Different ways of applying this rule repeatedly can yield different results.


## ► Karnaugh maps

- Systematic and visual method for combining minterms.
  - Invented by Edward Veitch in 1952
  - Refined by Maurice Karnaugh in 1953
- Idea:
  - **map** all minterms on a 2D grid
  - **neighbourhoods** in the grid indicate which terms can be combined.
- Works well for 2, 3 or 4 variables.
- More variables: use algorithm by Quine/McCluskey (out of the scope of this module)

# ► Karnaugh maps

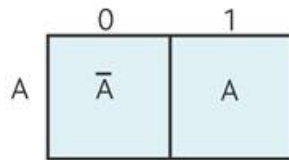

(a) One-variable Karnaugh map.

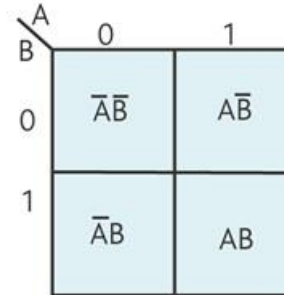

(b) Two-variable Karnaugh map.



# ► Karnaugh maps

	0	1
A	$\bar{A}$	A

(a) One-variable Karnaugh map.

		0	1
A	B		
0		$\bar{A}\bar{B}$	$A\bar{B}$
1		$\bar{A}B$	$AB$

(b) Two-variable Karnaugh map.

		00	01	11	10
AB	C				
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

(c) Three-variable Karnaugh map.

# ► Karnaugh maps

	0	1
A	$\bar{A}$	A

(a) One-variable Karnaugh map.

		0	1
A	B		
0		$\bar{A}\bar{B}$	$A\bar{B}$
1		$\bar{A}B$	$AB$

(b) Two-variable Karnaugh map.

		AB	00	01	11	10
C						
0			$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1			$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

(c) Three-variable Karnaugh map.

			AB	00	01	11	10
CD							
00				$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}B\bar{C}\bar{D}$	$AB\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$
01				$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$AB\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$
11				$\bar{A}\bar{B}CD$	$\bar{A}BCD$	$ABCD$	$A\bar{B}CD$
10				$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$AB\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$

(b) Four-variable Karnaugh map.

## ► Structure of Karnaugh maps



AB \ C	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}C$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

AB \ CD	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}B\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}C\bar{D}$
01	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$A\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$
11	$\bar{A}\bar{B}CD$	$\bar{A}BCD$	$ABCD$	$A\bar{B}CD$
10	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$ABC\bar{D}$	$A\bar{B}C\bar{D}$

- Subsequent labels for columns/rows differ in exactly 1 bit:  
 $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00$
- As a result, neighbouring cells differ in exactly one bit, i.e. minterms only differ in one negation (e.g.  $A\bar{B}\bar{C}$  vs.  $ABC$ ).

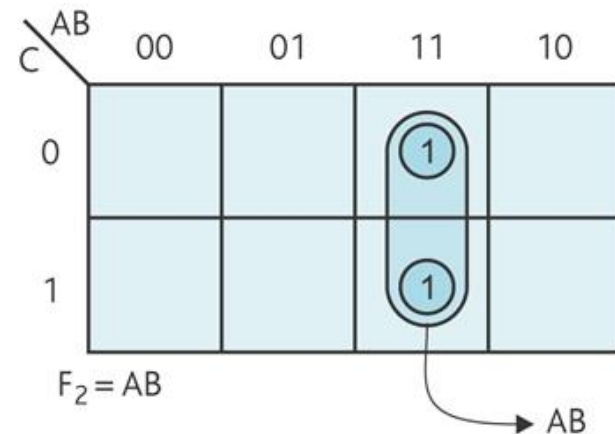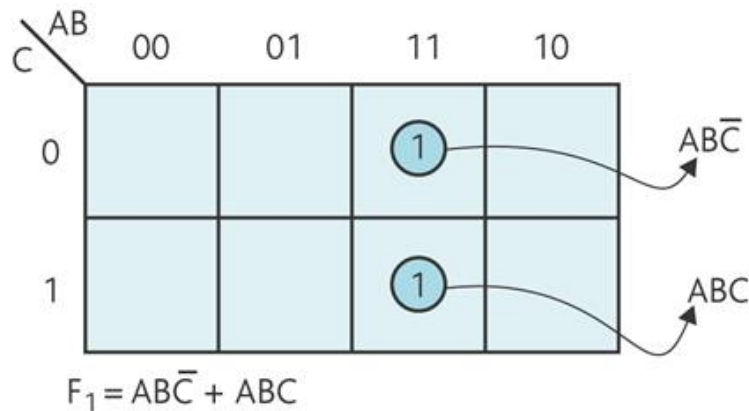
## ► Karnaugh maps

- A Karnaugh map works like a truth table.
- Typically truth values 1 are written down, empty cells are read as 0.
- Neighbouring 1s can be combined to give a simpler formula.



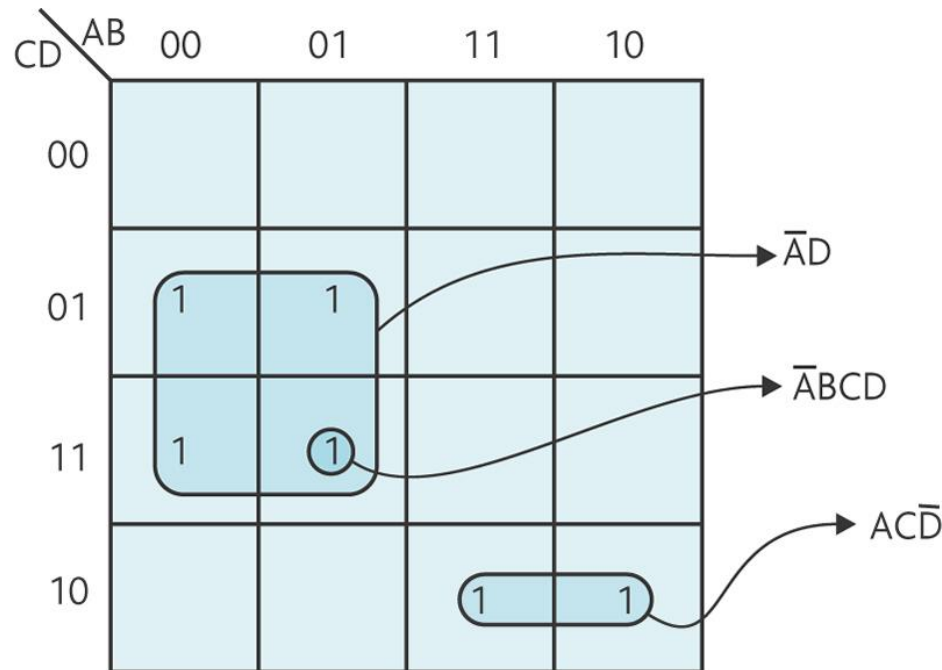
## ► Karnaugh maps: rectangles

- Also works for larger rectangles if **side lengths** are **1,2, or 4**.
- Larger rectangles have less variables.




## ► How to use Karnaugh maps

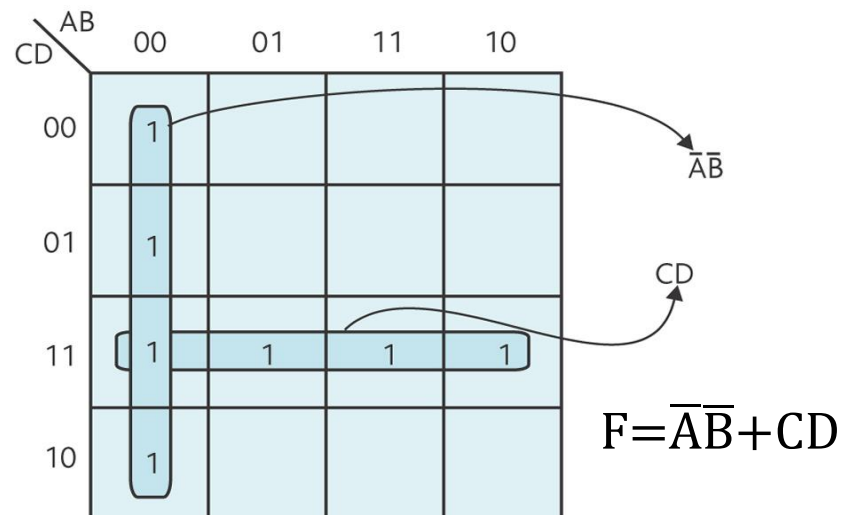1. Enter all 1s according to the function to be simplified.
2. Draw rectangles with side lengths 1, 2, or 4 as to:
  - **cover all 1s and no empty cells (0s)** (to represent the function)
  - using as **few rectangles** as possible ( $\rightarrow$  few sums)
  - make rectangles as **large** as possible ( $\rightarrow$  small products)
3. Read off product terms and simplified formula.
  - Recall: side lengths 1, 2, or 4 are OK; 3 isn't!
  - Rectangles may overlap.



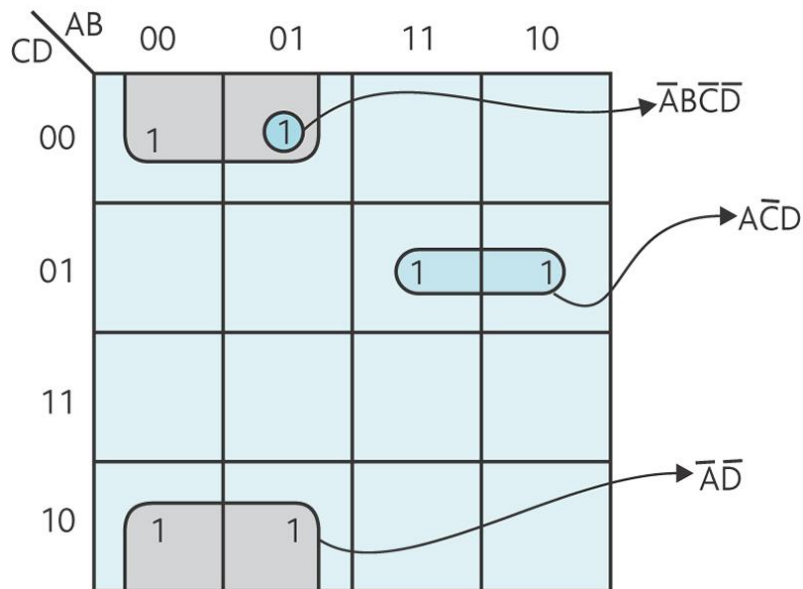
## ► Wrapping around

- **Caution:** neighbourhoods “wrap around” on all sides.



$$F = \bar{A}\bar{D} + \bar{A}\bar{C}D$$

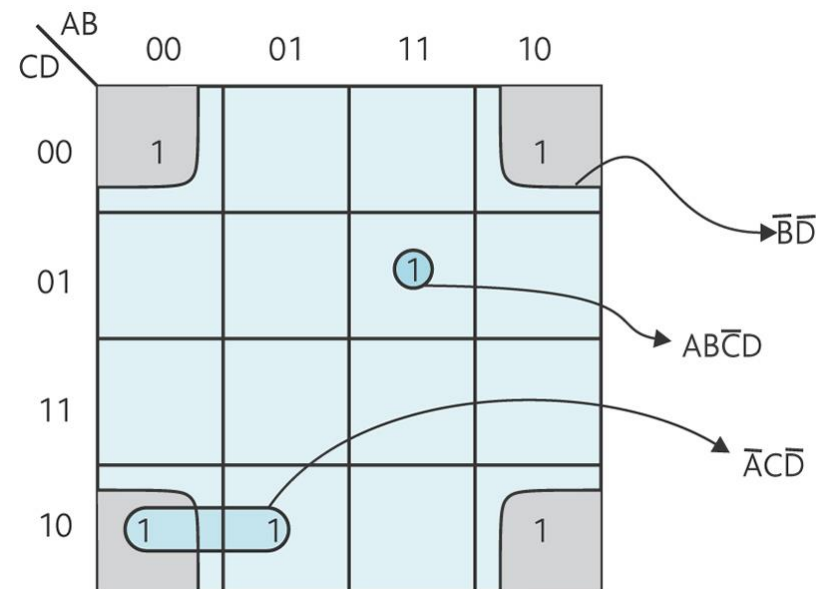

$$F = \bar{B}\bar{D} + AB\bar{C}\bar{D} + \bar{A}\bar{C}\bar{D}$$

## ► Example: Majority circuit

- Use a Karnaugh map to simplify

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$



## ► De Morgan's theorem

- Two further rules of Boolean algebra are collectively known as De Morgan's theorem:

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- In other words, to apply De Morgan's theorem to a Boolean function we change ANDs into ORs, change ORs into ANDs, and variables/literals are complemented.
- Example: Apply De Morgan's theorem to

$$F = \overline{X \cdot Y + X \cdot Z}$$

$$= \overline{X \cdot Y} \cdot \overline{X \cdot Z}$$

$$= (\overline{X} + \overline{Y}) \cdot (\overline{X} + \overline{Z})$$

## ► Implementing in NAND and NOR only

- De Morgan's theorem is important because it allows:
  - an AND gate to be implemented by an OR gate and an inverter;
  - an OR gate to be implemented by an AND gate and an inverter.
- Hence any device that can be made from a combination of ANDs, ORs and NOTs can be made using a combination of NANDs (or NORs) only.
- This is of practical value because NAND gates operate at higher speed than AND gates, and require fewer components at the chip level.

## ► Example: implementing in NAND/NOR

- Recall the majority device  
 $F = AB + BC + AC$



- We note that

$$F = \overline{\overline{F}} = \overline{\overline{AB + BC + AC}}$$

- Now apply De Morgan:

$$F = \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{AC}}$$

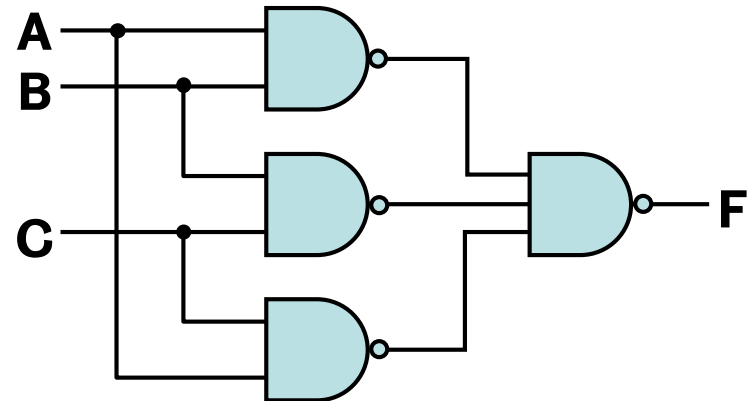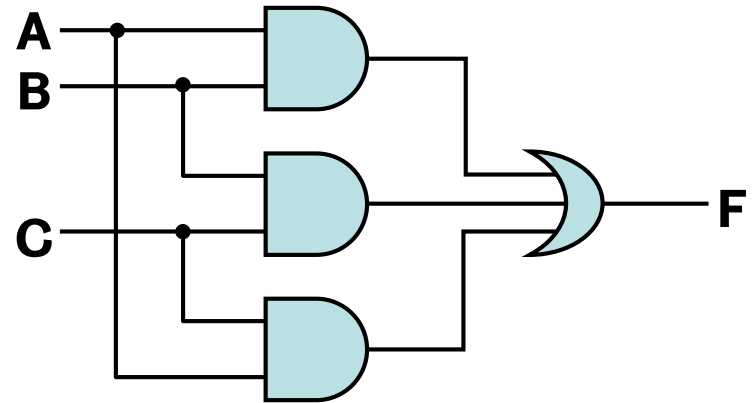- ❓ **Exercise: use a truth table to verify that the two circuits are equivalent**



## ► Summary

- Boolean algebra provides a powerful means of describing and simplifying logic devices.
- Karnaugh maps visualise terms that can be grouped, leading to Boolean formulas with less and shorter terms than the canonical S-of-P form.
- De Morgan's theorem is important because it suggests a means by which any digital circuit can be implemented in NAND and NOR logic only.